


- Need charge pump circuit \rightarrow -5 V \rightarrow Op-Amp

- Voltage follower circuit before DC bias? ✓


- Impedance mismatch

Prototype Schematic

Input Stage

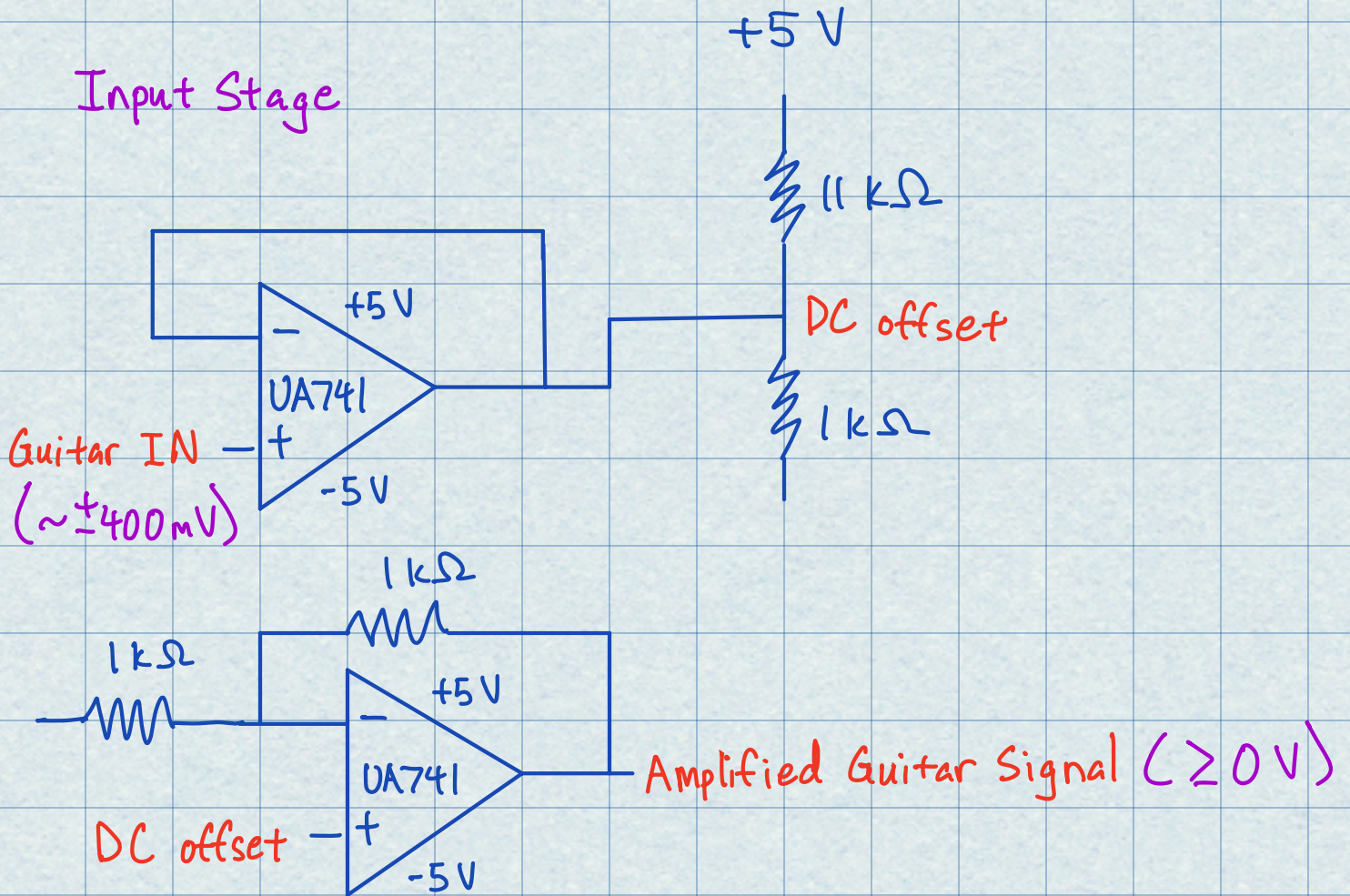

Power system

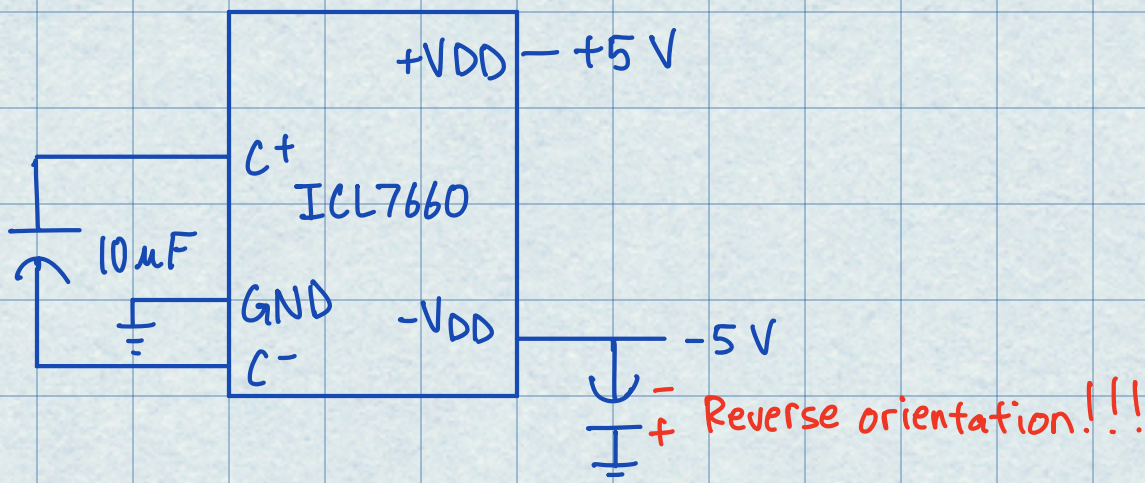

Output Stage

